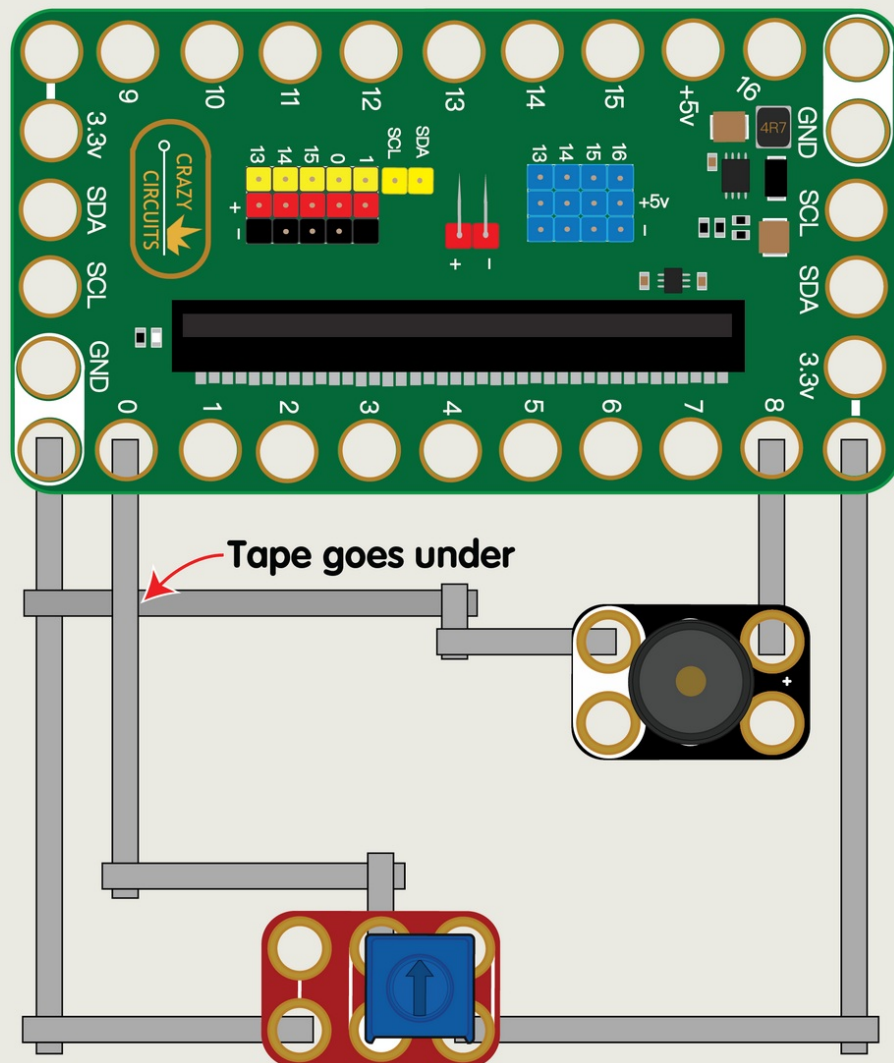




# CH16-D - Potentiometer Piezo Chooser

Connect a Potentiometer to a Bit Board and control a Piezo with code.

Written By: Pete Prodoehl



# INTRODUCTION

Connect a Potentiometer to a Bit Board and control a Piezo with code.

We'll explore how we can make sounds using a piezo speaker with a potentiometer.



## TOOLS:


- [Computer](#) (1)
- [Scissors](#) (1)



## PARTS:


- [Crazy Circuits Bit Board](#) (1)
- [micro:bit](#) (1)
- [Maker Tape](#) (1)  
1/8" Wide
- [Crazy Circuits Potentiometer Chip](#) (1)
- [Crazy Circuits Piezo Speaker Chip](#) (1)
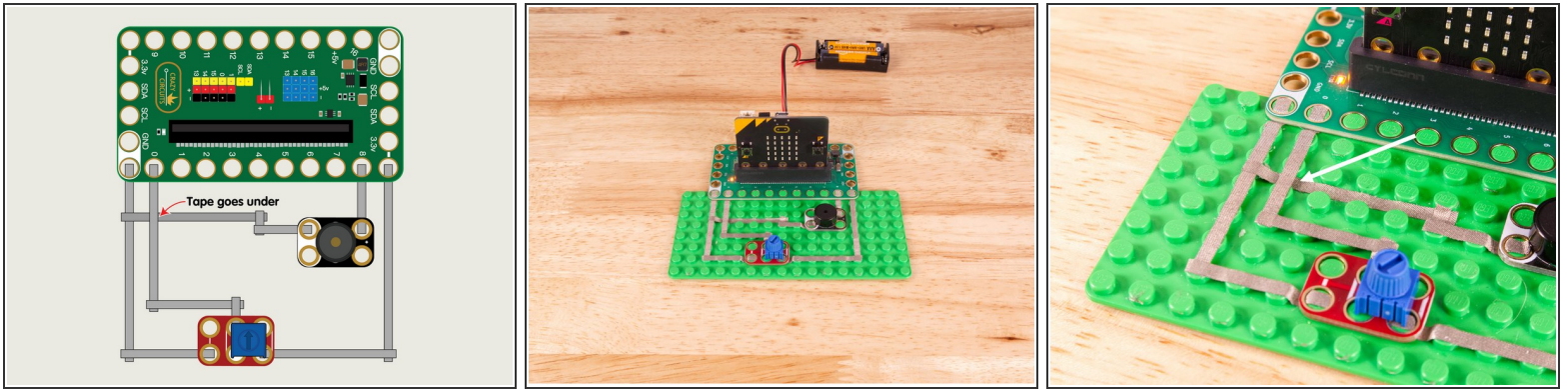
## Step 1 — Connect the Potentiometer and Piezo




- We'll use **Maker Tape** to connect the Potentiometer and the Piezo to the Bit Board on a LEGO baseplate.
- The Piezo will connect to **Pin 8** and to **Ground (GND)** **BUT!** We're going to use the "gutter" between the LEGO baseplate studs so we can have **two layers of tape** that do not touch.
  - See the photos to show how this works. It's a technique we'll use for certain projects. It can also be used when you're tight on space for tape paths.
- Once the Piezo is connected we'll need to connect the Potentiometer. One side goes to **Ground (GND)** and the other side to **3.3v**
- We will then connect the center of the Potentiometer to **Pin 0**. (Note that **Pin 0** is an **analog** pin.)
- ☑ You'll notice the **Ground** on the Bit Board (as well as the Potentiometer, Piezo, and other Crazy Circuits components we'll use) is color coded **White**.
- ☑ The **3.3v** hole on the Bit Board is labeled and is actually two holes right next to each other on the Bit Board. (There is a small line showing the connection between them.)

## Step 2 — Load the Code

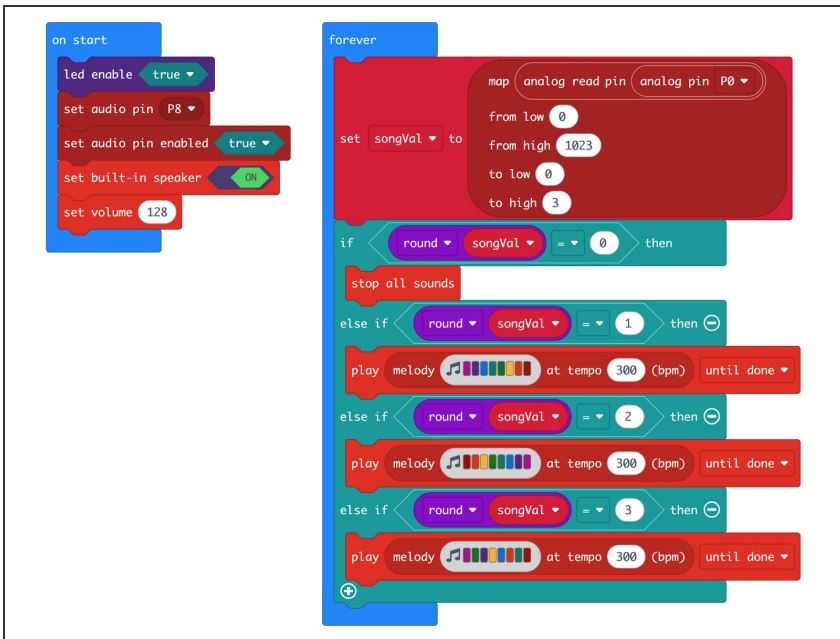


- If you've never used a micro:bit before you'll want to check out this guide: [Bit Board V2 Setup and Use](#)
- We're going to load the following code for our **Potentiometer Piezo Chooser** program: [https://makecode.microbit.org/\\_gCvJ9FeyK...](https://makecode.microbit.org/_gCvJ9FeyK...)
- ⚠ The micro:bit (since the release of version V2) has included a built-in piezo speaker on the back. You can use the built-in Piezo on a V2 micro:bit or connect a Crazy Circuits Piezo with Maker Tape as we've shown in this guide.
- The micro:bit will play a different melody depending on the position of the Potentiometer dial.
- We're mapping the Potentiometer input from a scale of **0-1024** to **0-3** for a total of four positions, one which is silent and three which will play sounds.

## Step 3 — Test it Out!

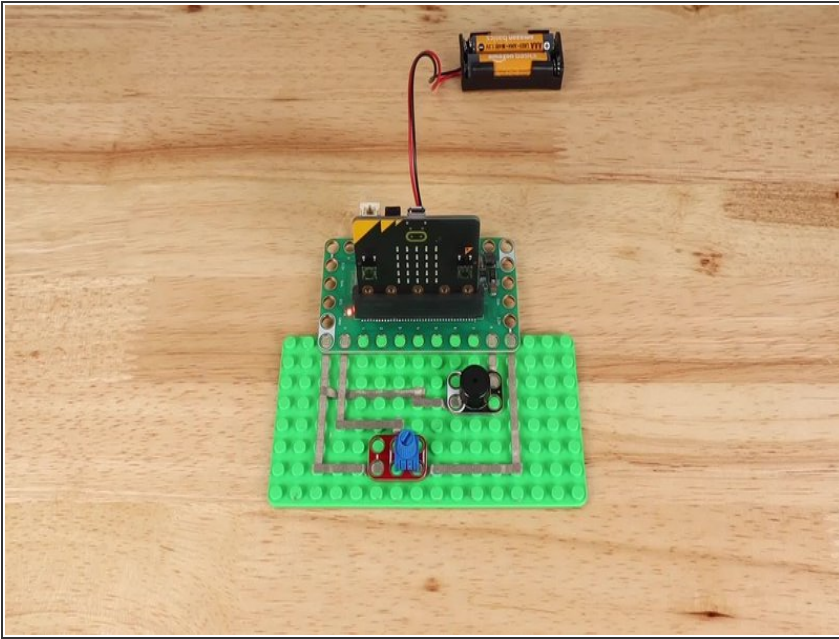

- Once the code is loaded it should start running immediately.
- ① You can power the micro:bit via the USB cable you used to load the code or you can use a battery pack plugged into the Bit Board.
- Start with the dial all the way to the left (0) and it will not play a sound. Move it clockwise slowly and you'll hear different melodies played.

## Step 4 — Follow Along

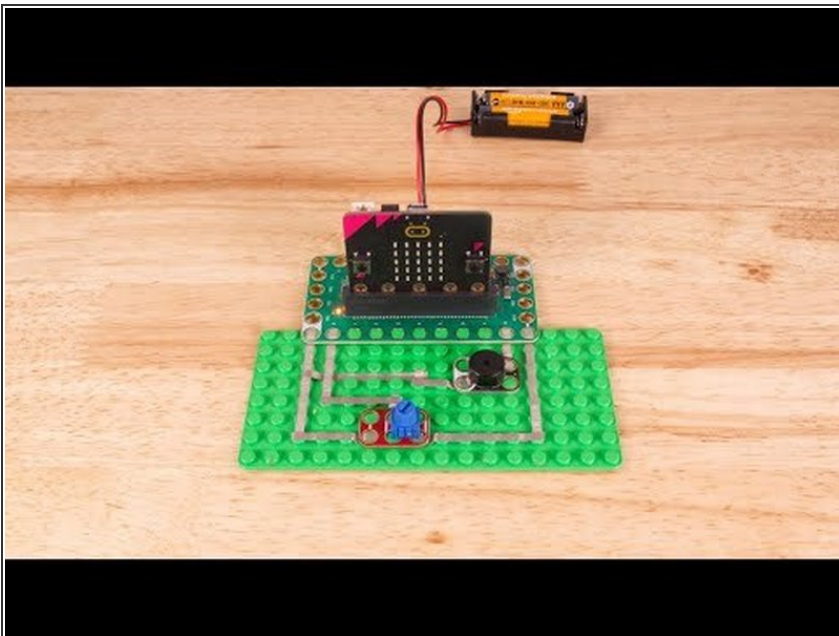

- Follow along with our recorded Live Stream!
- ① You can watch the full video of us walking through this project, along with explaining and exploring the code: <https://youtube.com/live/g6-AnKVkcFk>