
Paper Circuits Lesson Day 2: Parallel vs. Series Circuits

Written By: Joshua

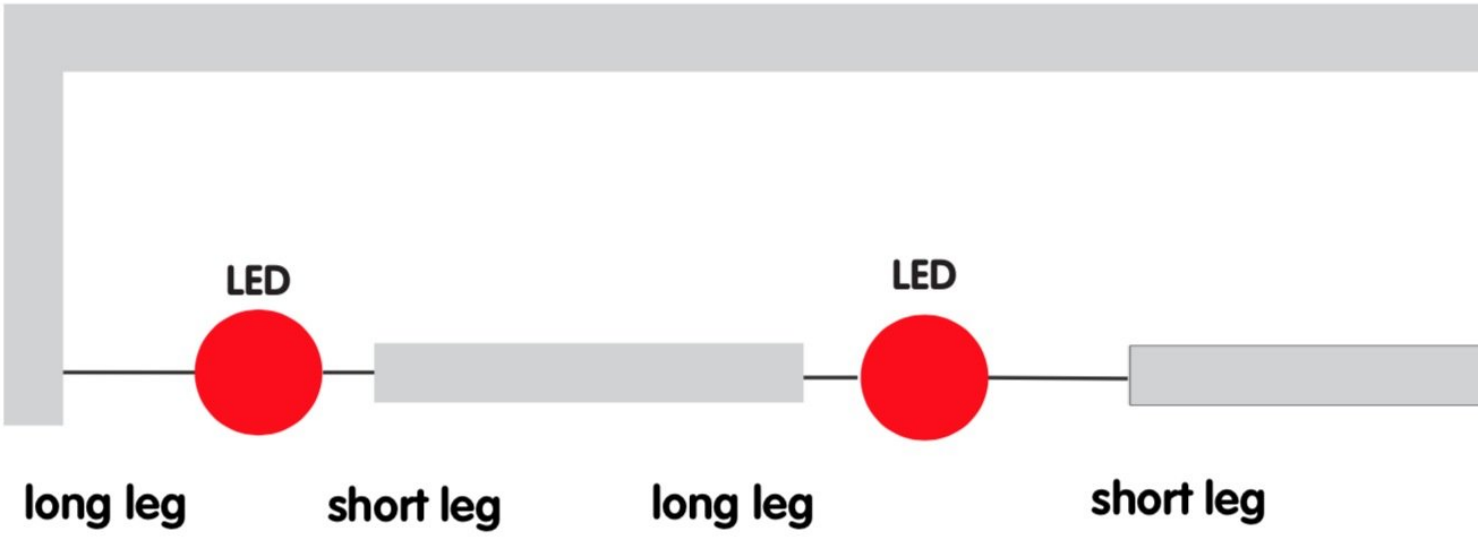

INTRODUCTION

Learn about the differences in Parallel and Series circuits with this STEM lesson. Below you'll find a lesson plan as well as student activity pages.

TOOLS:

- Scissors (1)

PARTS:

- Paper Circuits Kit (1)

© 2024