
Capacitive Touch Transistor Circuit

Create a simple transistor paper craft circuit that only turns on when your hands contact specific parts of the finished card. Trick your friends!

Written By: Andy Wallus

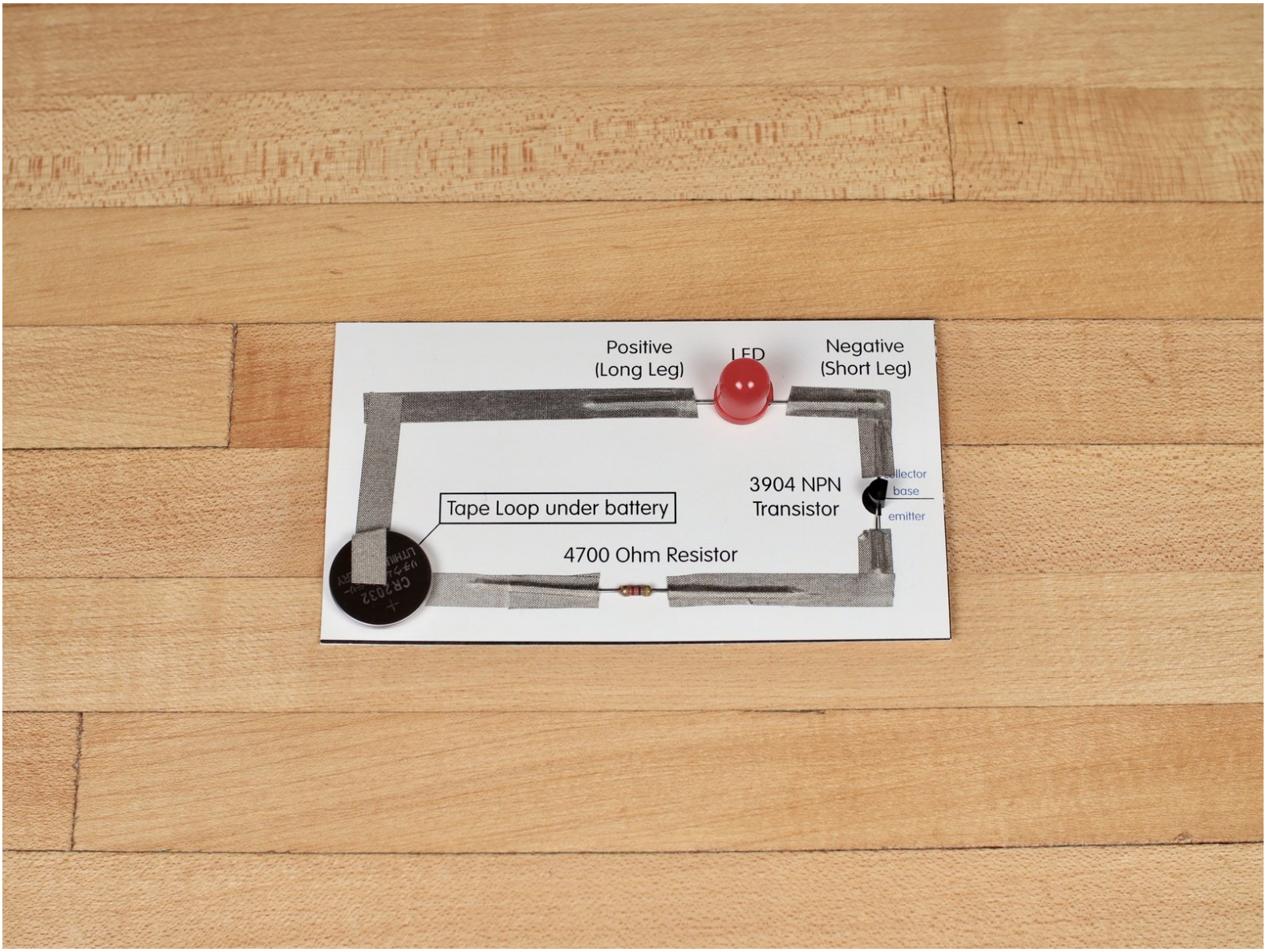

INTRODUCTION

Create a simple transistor paper craft circuit that only turns on when your hands contact specific parts of the finished card. Trick your friends!

TOOLS:

- Scissors (1)

PARTS:

- Maker Tape (1)
  1/4" Wide
- 2N3904 NPN Transistor (1)
- Jumbo 10mm Diffused LED (1)
- 4700 Ohm Resistor (1)
- CR2032 Battery (1)

© 2024

When finished, this circuit card only tuns on when the user contacts a hidden transistor base wire AND the positive tape path at the same time.

© 2024