Solar Cell with LED Paper Circuit

Use a small solar cell as the voltage source in this simple LED circuit.

Written By: Andy Wallus



TOOLS:

- Scissors (1)

PARTS:

- Maker Tape (1)
  1/4" Wide
- Jumbo 10mm Diffused LED (1)
- Printable Template (1)
- 2V Solar Cell (1)

© 2024

Convert solar energy into electrical energy with this simple paper circuit!

© 2024