
Paper Circuits Lesson: Morse Code

Use this printable template and a few basic materials to create a simple Morse Code encoder. Send silent messages to all your friends afterward!

Written By: Andy Wallus

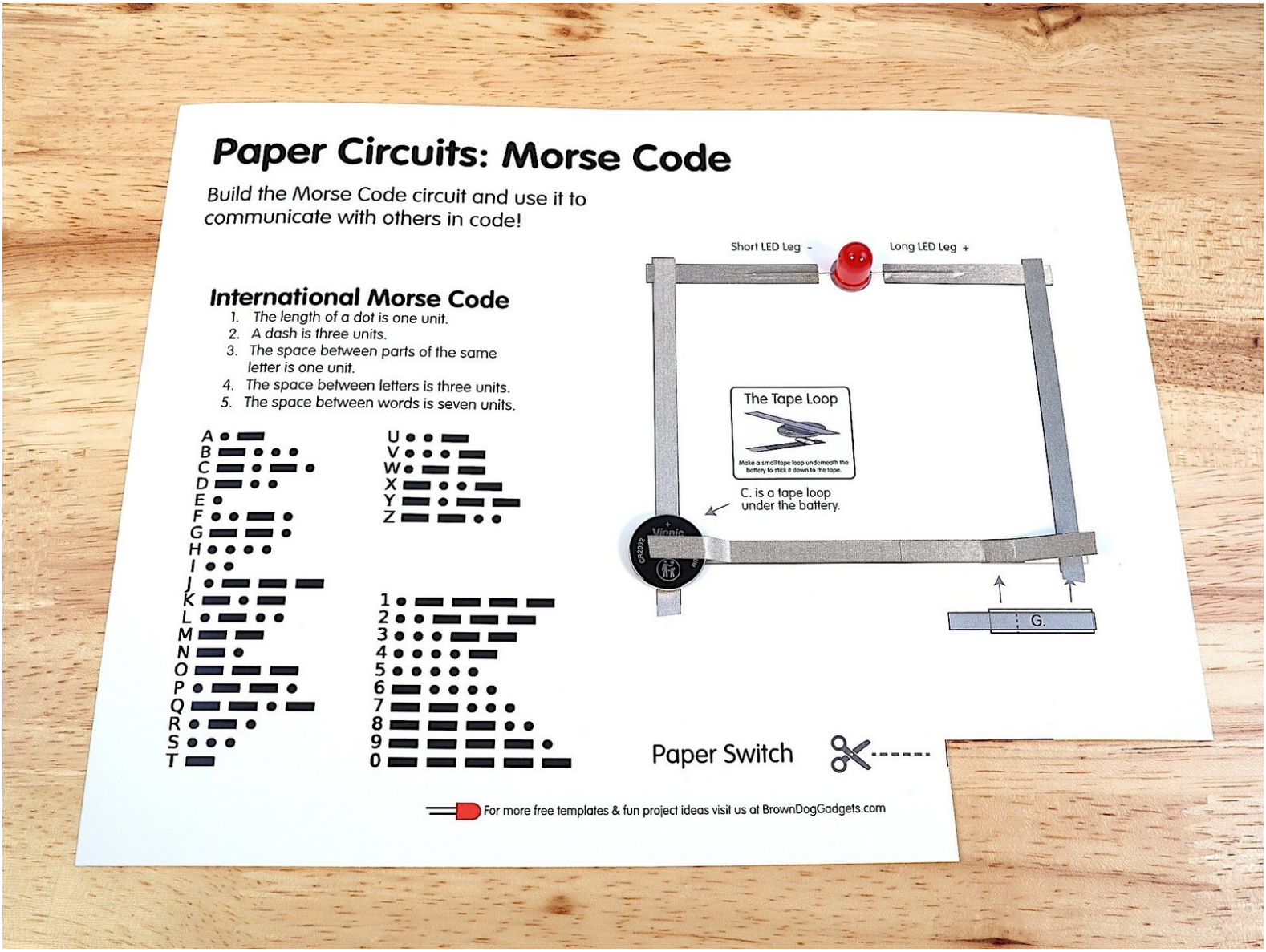

INTRODUCTION

Use this printable template and a few basic materials to create a simple Morse Code encoder. Send silent messages to all your friends afterward!

TOOLS:

- Scissors (1)

PARTS:

- Jumbo 10mm Diffused LED (1)
- Maker Tape (1)
  1/4 Wide
- CR2032 Battery (1)
- Printable Template (1)

© 2024

After finishing the circuit, use it to send messages!

© 2024