Picture You and Me Together Valentine's Card

Create a fun light-up card for Valentine's Day. Just add an LED, a CR2032 battery, and some Maker Tape.

Written By: Pete Prodoehl



INTRODUCTION

Create a fun light-up card for Valentine's Day. Just add an LED, a CR2032 battery, and some Maker Tape.

TOOLS:

- Scissors (1)


PARTS:

- Paper Circuits Kit (1)

© 2024

Step 1 — Make Your Card



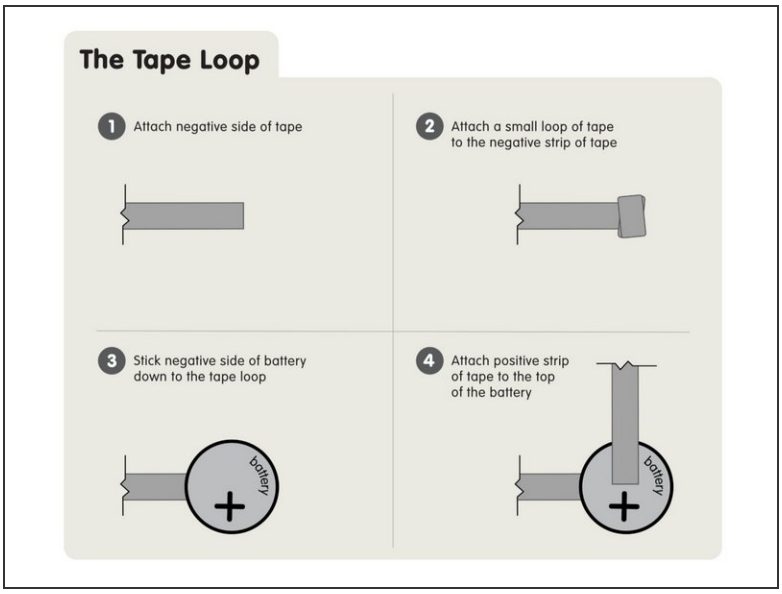

- In general build this project in this order:
  - Print out the full-color card, or print out the black and white card, and color/decorate as desired.
  - Poke holes through front for LED legs, then push legs through front.
  - On inside of card, bend legs down flat against paper.
  - Add Maker Tape and battery to complete your circuit.

ⓘ Note: If you are using thicker paper (such as cardstock) we recommend using a large safety pin to poke the holes in the paper to put the LED legs through.

Enjoy your card!