
Day 1: Resistance Isn't Futile

Assemble a circuit with new components; primarily fixed resistors and investigate their effects on light-based outcomes in that circuit.

Written By: Andy Wallus

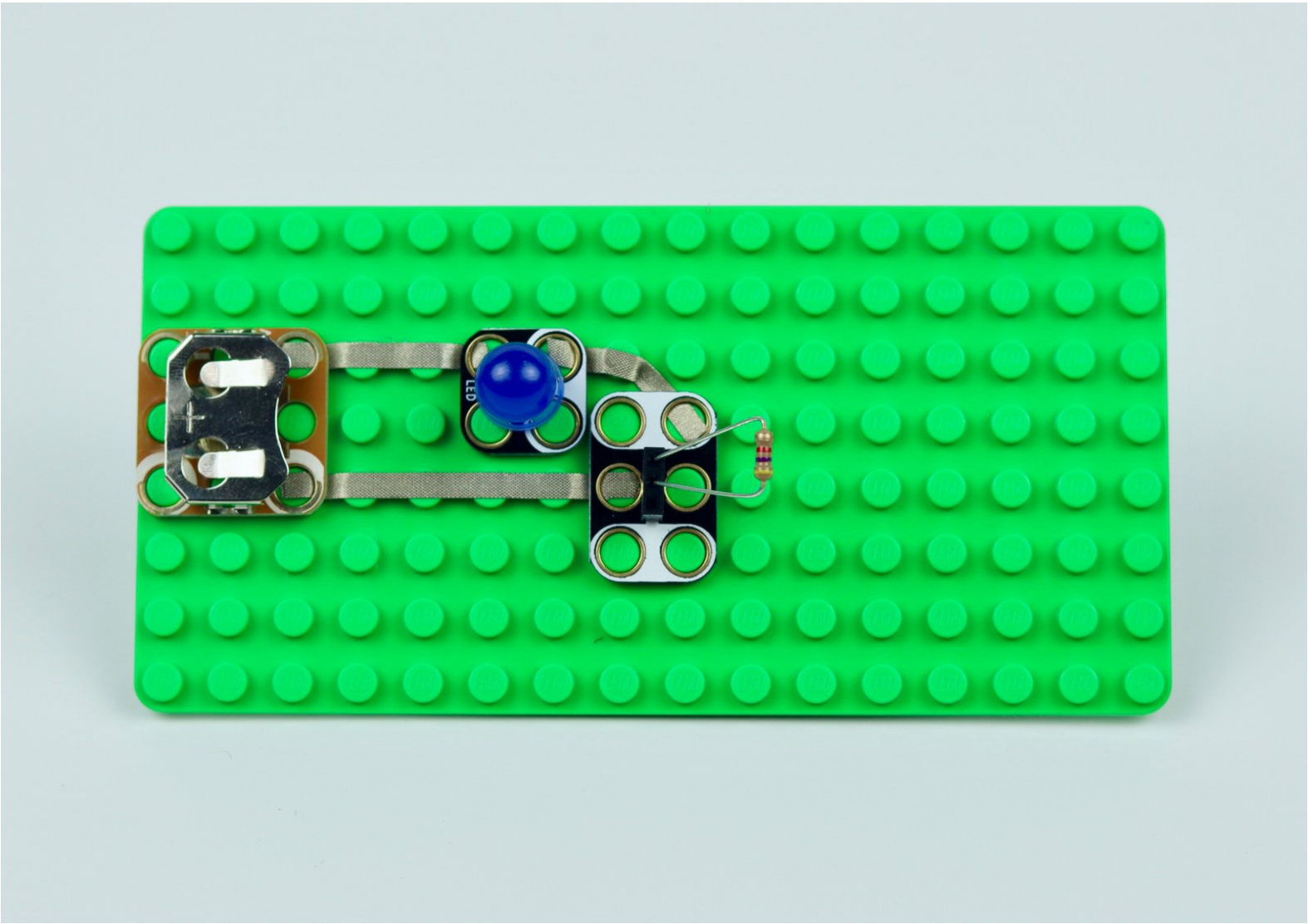

INTRODUCTION

Assemble a circuit with new components; primarily fixed resistors and investigate their effects on light-based outcomes in that circuit.

TOOLS:

- Scissors (1)

PARTS:

- Crazy Circuits Classrooms: Circuits 101 (1)

Students should now know what resistance is, how it affects light, where it comes from and how we use it as a control element in circuitry.

© 2024