
Day 3: Parallel and Series

Explore circuits that allow more than one component to work at the same time. Physically assemble and observe both parallel and series circuits from kit.

Written By: Andy Wallus

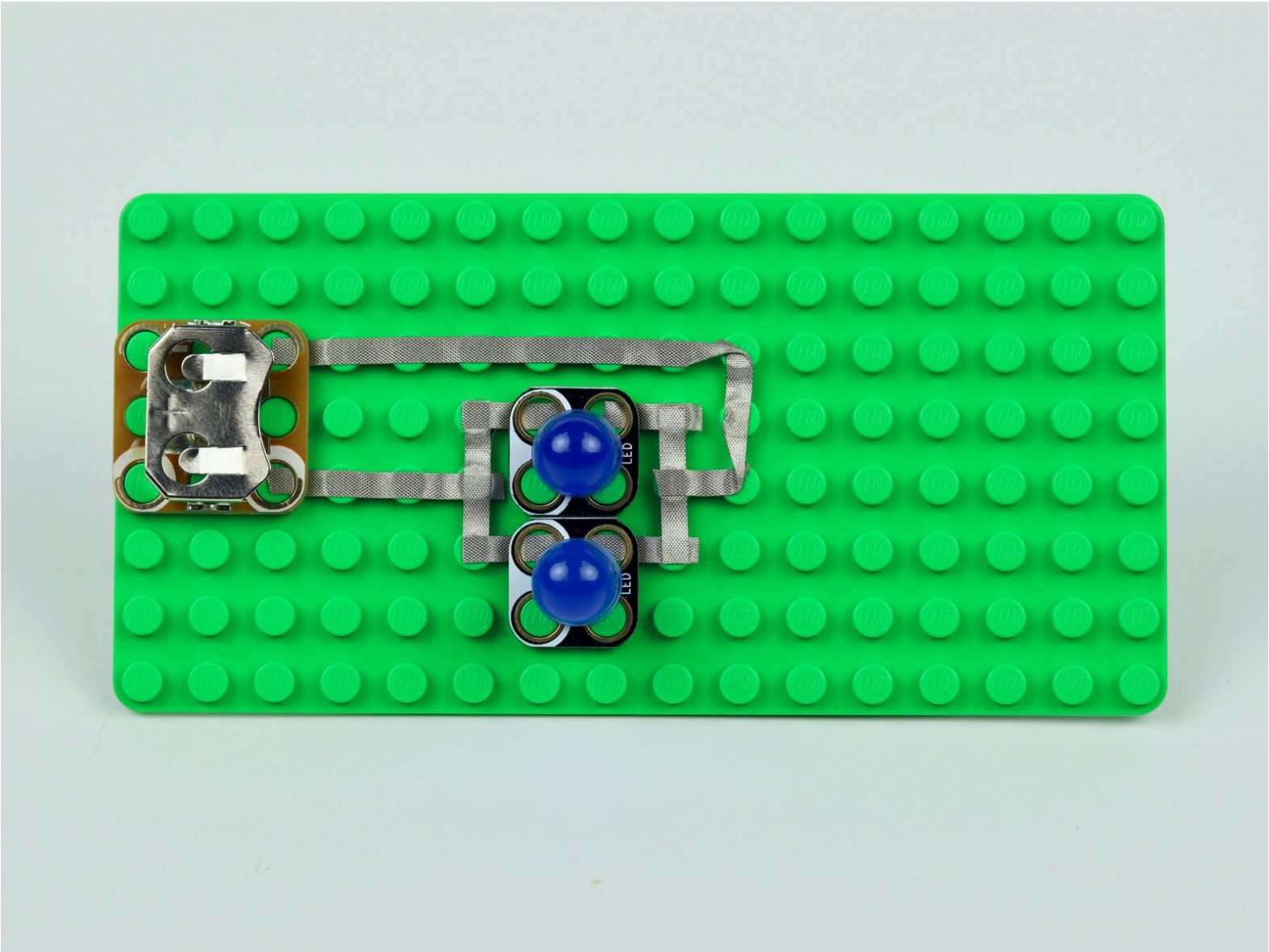

INTRODUCTION

Explore circuits that allow more than one component to work at the same time. Physically assemble and observe both parallel and series circuits from kit.

TOOLS:

- Scissors (1)

PARTS:

- Crazy Circuits Classrooms: Circuits 101 (1)

Students will have assembled a circuit that requires two simultaneous outcomes in two basic forms; series and parallel. Through observation, they will also have begun to understand their characteristics, benefits and limitations.