
Day 2: Red Light, Green Light!

Assemble a circuit that uses switch polarity to allow selective control of two lights. Synthesize prior understandings and build a more complex outcome!

Written By: Amanda Etim

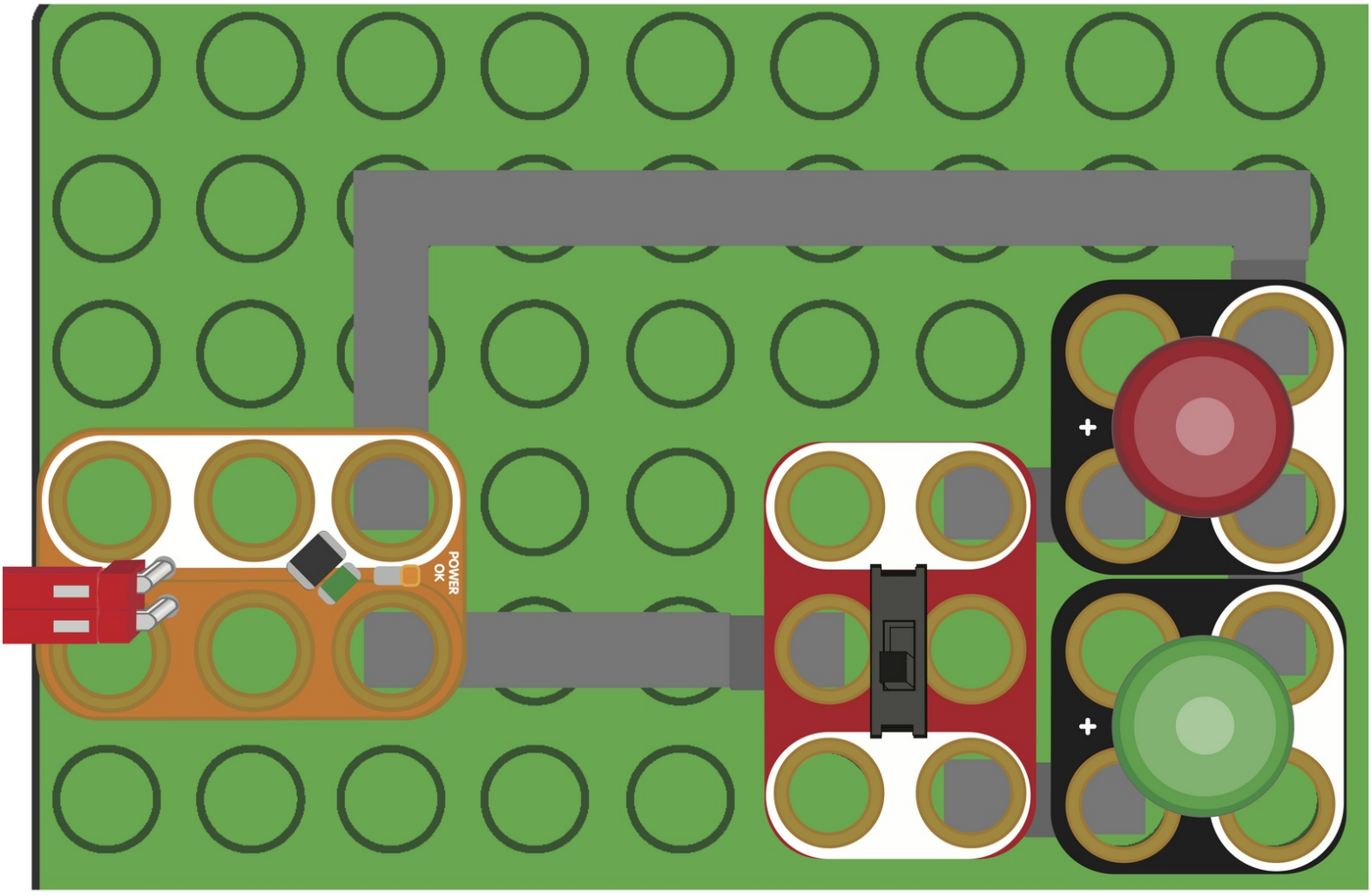

INTRODUCTION

Assemble a circuit that uses switch polarity to allow selective control of two lights. Synthesize prior understandings and build a more complex outcome!

TOOLS:

- Scissors (1)

PARTS:

- Crazy Circuits Classrooms: Circuits 101 (1)

© 2026