Day 5: Parallel and Series Circuit Arrangements

Full lesson plan, diagram set and assessment tools for Day 5 of Week 2 of the Circuits 101 classroom curriculum.

Written By: Andy Wallus

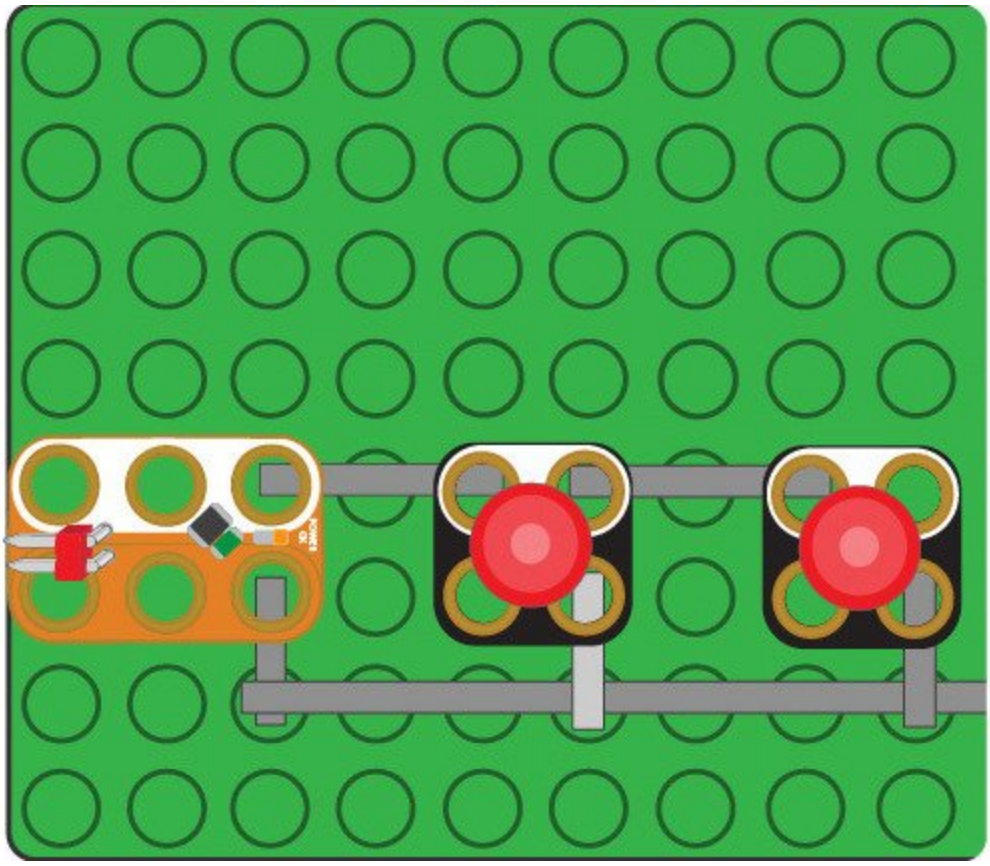

TOOLS:

- Scissors (1)
- Writing Utensils (1)

PARTS:

- Crazy Circuits Classrooms: Circuits 101 (1)
- AA Batteries (2)

per group

- Printable Lesson Plan (1)
- Printable Student Sheet (1)

per student

After this lesson your students will have assembled two different circuit arrangements that include multiple outcomes to see their similarities and differences.

© 2026